

①

Date:

Page:

In general for any bus transfer system:

K register of n bits can be multiplexed to produce an n-line common bus, where:

- n muxs are needed (= bit numbers)

no of inputs register → The size of each MUX is $K \times 1$ (= number of register)
 - W selection lines are needed where, $2^W \geq K$

* Selection line = \log_2 inputs

↳ $\log_2 \text{ muxs}$

example: for register R₀ to R₆₃ in a 16 bit bus system; what is the mux size we use? and How many select bits are needed?

$$\text{Size} = 64 \times 1 = 64$$

$$\text{no of muxs} = 16$$

$$\text{no of selection line} \Rightarrow 2^4 \Rightarrow 4$$

Memory Transfer:

The read operation is the transfer of information from a memory word to the outside environment: $DR \leftarrow M[AR]$

Data register ← address register

The write operation: is the transfer of new information to be stored into a memory word $M[AR] \leftarrow R1$

What is memory word? address of data in memory

- Computer Microoperations

- Arithmetic microoperations

- Arithmetic addition and subtraction

Microoperation:- The operations on the data in registers



Computer microoperations 3 types:

1- Arithmetic 2- Logic 3- Shift

Arithmetic microoperations

Symbolic designation	Description
$R3 \leftarrow R1 + R2$	Contents of R1 Plus R2 Transferred to R3
$R3 \leftarrow R1 - R2$	~ ~ R1 Minus R2 ~ ~ R3
$R2 \leftarrow \overline{R2}$	1's Complement The contents of R2
$R2 \leftarrow \overline{R2} + 1$	2's ~ ~ ~ (negative)
$R3 \leftarrow R1 + \overline{R2} + 1$	<div style="border: 1px solid black; padding: 5px; display: inline-block;"> $R1$ Plus The 2's Complement of R2 (Subtract) </div>
$R1 \leftarrow R1 + 1$	Increment R1 by one
$R1 \leftarrow R1 - 1$	Decrement ~ ~ ~

Arithmetic addition: $R3 \leftarrow R1 + R2$ Arithmetic Subtraction: $R3 \leftarrow R1 - R2$

$$* R3 \leftarrow R1 + (R2' + 1), \text{ 2's Complement } = R1 - R2$$

$$* R1 - R2 \text{ (بالإضافة إلى 2's Complement إلى 1) } \rightarrow R1 - R2$$

Steps: $R2'$ is The Complement of R2

- Adding 1 to The 1's Complement of R2 gives The 2's Comp. of R2

- Adding R1 to the 2's Comp. of R2 is equivalent to

Subtracting R2 from R1

③

Page:

Date:

example "مثال" $R1 = 1000$
 $R2 = 1101 +$

$$\begin{array}{r} 10101 \\ \underline{2} \end{array} = R1 + R2$$

$[R1 - R2]??$

① find $R2' = 0010 \rightarrow 1's \text{ Complement}$

② add 1 to $R2'$ $\rightarrow 2's \text{ Complement}$

$$\begin{array}{r} 0010 \\ \underline{1} \end{array} +$$

$$R2' + 1 = 0011 \rightarrow 2's \text{ Complement}$$

③ add $R1$ to $R2' + 1$


$$\begin{array}{r} R1 \quad 1000 \\ R2' + 1 \quad 0011 \\ \hline \end{array} +$$

$$1011 = R1 - R2$$


Arithmetic hardware implementation

- ① 4-bit binary adder
- ② 4-bit binary adder-subtractor
- ③ 4-bit binary incrementer

For reminding

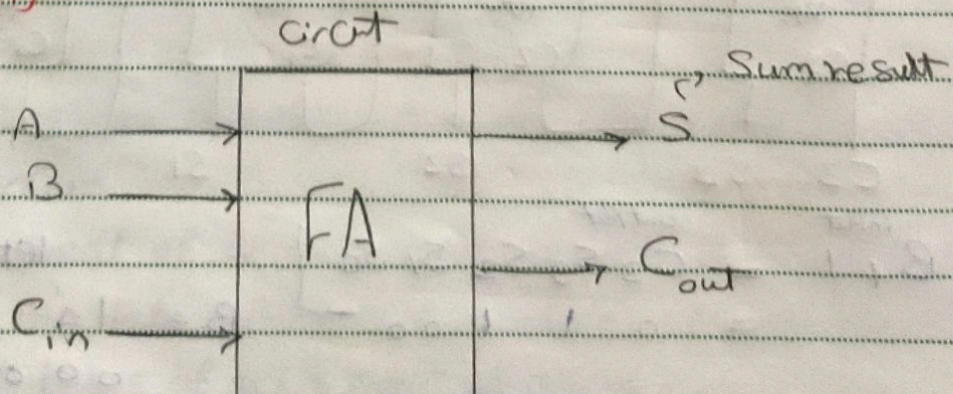

① 4-bit binary adder

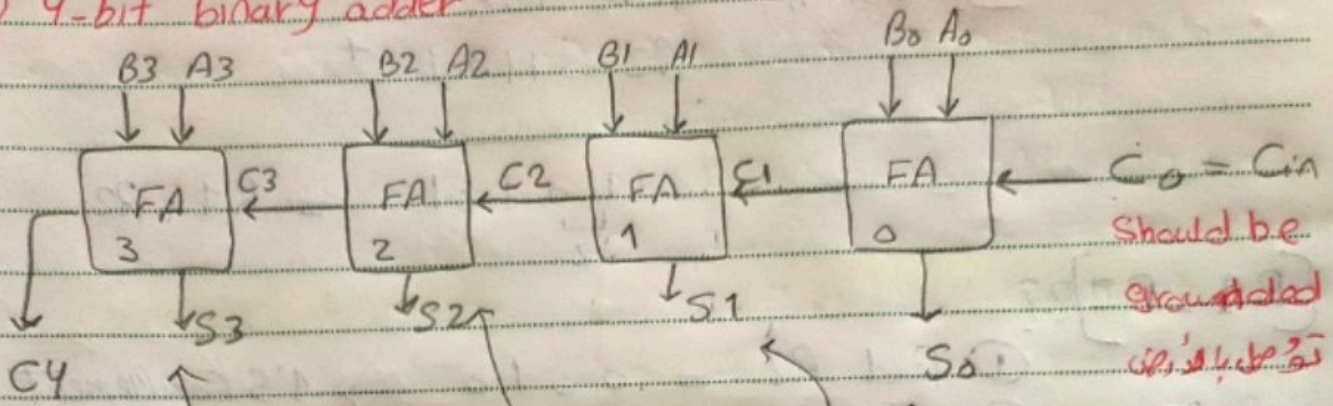

Note → No. of FA = No. of bits

Let

$$A = A_3 A_2 A_1 A_0 = 1010$$

$$B = B_3 B_2 B_1 B_0 = 0010$$


* Cout of FA1 → Cin of FA2

$$\text{Sum} = A + B = \begin{array}{r} 1010 \\ 0010 \\ \hline 01100 \end{array}$$

$C_4 \leftarrow S_3 \leftarrow S_2 \leftarrow S_1 \leftarrow S_0$

② 4-bit binary incrementor

$B = B_3 B_2 B_1 B_0$

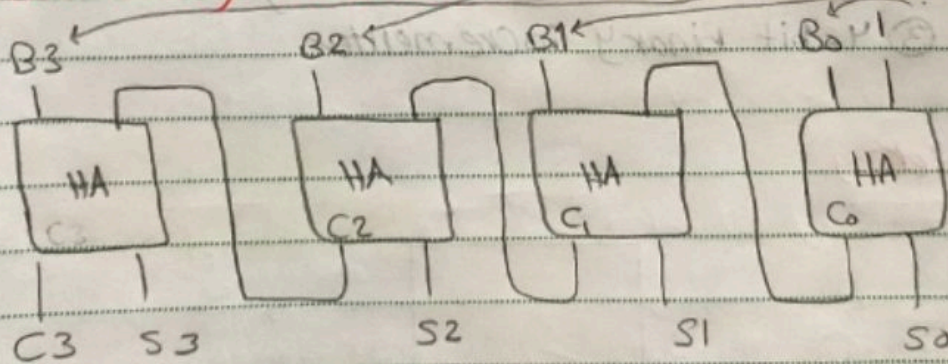

input

$$B + 1 = C_3 S_3 S_2 S_1 S_0$$

output

$$= 01100$$


let

$$B = 1011$$


$$\begin{array}{r} 1011 \\ 0001 \\ \hline 01100 \end{array}$$

Date:


Remind 11

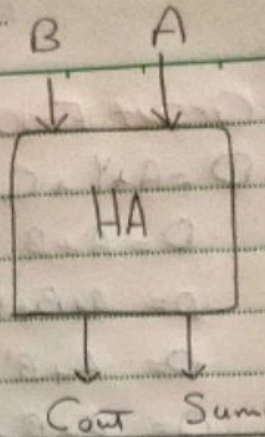

③ 4-bit binary adder-subtractor

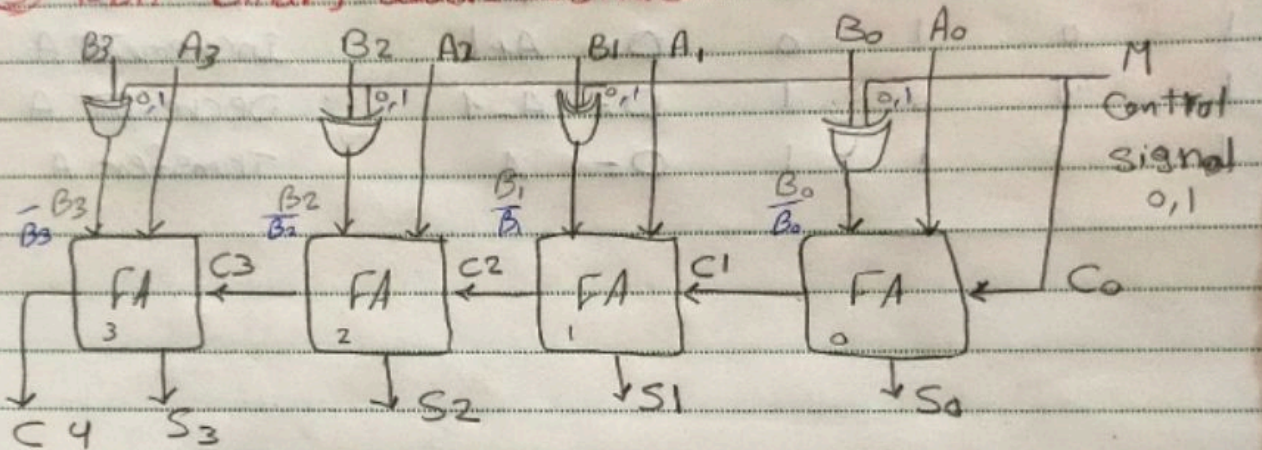

advantages of XOR gate

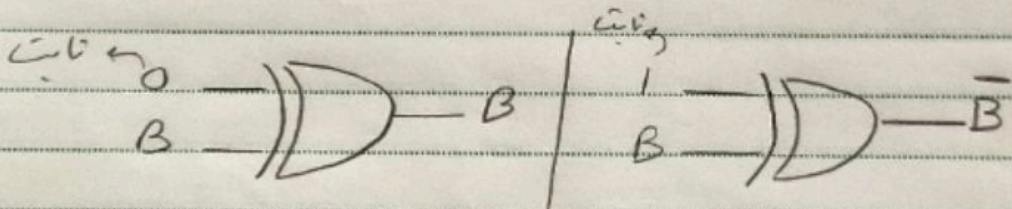

at

$$m = 0 \rightarrow \text{Sum } A + B, \quad m = 1 \rightarrow A_0 + \bar{B}_0 + 1 = A_0 - B_0$$

Arithmetic Circuit

- The arithmetic micro operations can be implemented in one composite arithmetic circuit.
- The basic component of an arithmetic circuit is the parallel adder.
- By controlling the data inputs to the adder, it is possible to obtain different types of arithmetic operations.
- The output of binary adder is calculated from arithmetic sum.

$$D = A + Y + C_{in}$$

⑥

Date:

Page:

Arithmetic Circuit Function

S_1	S_0	C_{in}	Y	$D = A + Y + C_{in}$	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with Carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A