
 


CHAPTER 4

4.1

 

4.2



T_0	T_1	T_2	T_3	S_1	S_0	R_3	load
0	0	0	0	X	X	0	
1	0	0	0	0	0	1	
0	1	0	0	0	1	1	
0	0	1	0	1	0	1	
0	0	0	1	1	1	1	

$$S_1 = T_2 + T_3$$

$$S_0 = T_1 + T_3$$

$$\text{load} = T_0 + T_1 + T_2 + T_3$$

4.3

P: $R1 \leftarrow R2$

P'Q: $R1 \leftarrow R3$

4.4

Connect the 4-line common bus to the four inputs of each register.

Provide a "load" control input in each register.

Provide a clock input for each register.


To transfer from register C to register A:

Apply $S_1S_0 = 10$ (to select C for the bus.)

Enable the load input of A

Apply a clock pulse.

4.5

 


4.6

- (a) 4 selection lines to select one of 16 registers.
- (b) 16×1 multiplexers.
- (c) 32 multiplexers, one for each bit of the registers.


4.7

- (a) Read memory word specified by the address in AR into register R2.
- (b) Write content of register R3 into the memory word specified by the address in AR.
- (c) Read memory word specified by the address in R5 and transfer content to R5 (destroys previous value)


4.8

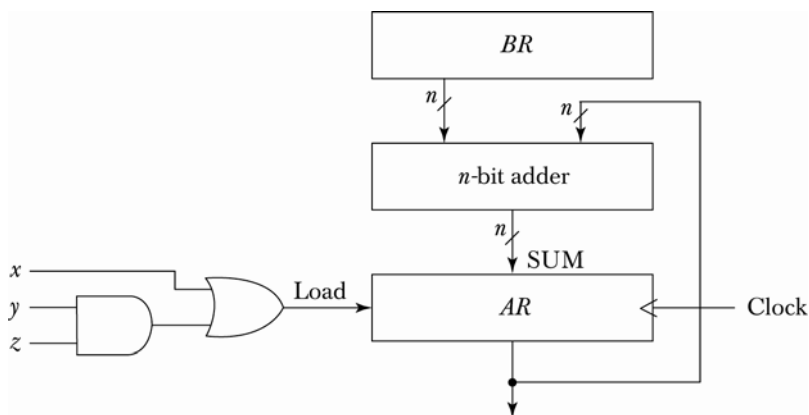


4.9

 

4.10

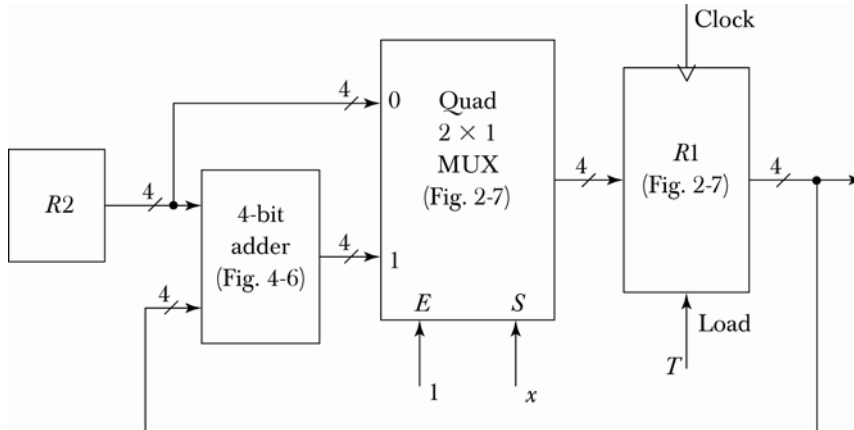

4.11

 

4.12

M	A	B	Sum	Cu
0	0111	+ 0110	1101	0
0	1000	+ 1001	0001	1
1	1100	- 1000	0100	1
1	0101	- 1010	1011	0
1	0000	- 0001	1111	0

$$7 + 6 = 13$$


$$8 + 9 = 16 + 1$$

$$12 - 8 = 4$$


$$5 - 10 = -5 \text{ (in 2's comp.)}$$

$$0 - 1 = -1 \text{ (in 2's comp.)}$$

 4.13 $A - 1 = A + 2\text{'s complement of } 1 = A + 1111$




4.14

 


4.15


S	Cin	X	Y	
0	0	A	B	(A + B)
0	1	A	0	(A + 1)
1	0	A	1	(A - 1)
1	1	A	\bar{B}	(A - B)

 

4.16

 

4.17

 

4.18

(a) $A = 11011001$
 $B = 10110100$
 $A \leftarrow A \oplus B$ 01101101

$A = 11011001$
 $B = 11111101$ (OR)
 11111101 $A \leftarrow A \vee B$

4.19

(a) $AR = 11110010$
 $BR = 11111111(+)$
 $AR = 11110001$ $BR = 11111111$ $CR = 10111001$ $DR = 1110$
 1010

(b) $CR = 10111001$ $BR = 1111 1111$
 $DR = 11101010$ (AND) $+1$
 $CR = 10101000$ $BR = 0000 0000$ $AR = 1111 0001$ $DR = 11101010$

(c) $AR = 11110001$ (-1)
 $CR = 10101000$
 $AR = 01001001$; $BR = 00000000$; $CR = 10101000$; $DR = 11101010$

4.20

$R = 10011100$
 Arithmetic shift right: 11001110
 Arithmetic shift left: 00111000 overflow because a negative number changed to positive.

4.21

$R = 11011101$
 Logical shift left: 10111010
 Circular shift right: 01011101
 Logical shift right: 00101110
 Circular shift left: 01011100

4.22

S = 1 Shift left

 $A_0 A_1 A_2 A_3 I_L$

$$\begin{array}{ccccccc}
 & & 1 & 0 & 0 & 1 & 0 \\
 & \swarrow & \swarrow & \swarrow & \swarrow & & \\
 H = & 0 & 0 & 1 & 0 & & \text{shift left}
 \end{array}$$

4.23

- (a) Cannot complement and increment the same register at the same time.
- (b) Cannot transfer two different values (R_2 and R_3) to the same register (R_1) at the same time.
- (c) Cannot transfer a new value into a register (PC) and increment the original value by one at the same time.